


## Lesson 2

# Design Entities

This lesson will introduce you to the design entity, which is the VHDL language construct for describing hierarchical hardware designs. Not everything will be explained here; some of the detail will be covered in subsequent lessons.

Glossary Find Copy Help Back



 


# The Design Entity

Design Entities

1 of 59


We're going to start by learning about the **design entity**. A **design entity** is used to describe a block of hardware.

 Let's begin with a simple example: an and-or-invert gate.



Glossary Find Copy Help Back



 

# The Design Entity

A **design entity** is divided into two parts: the **entity** and the **architecture**. The entity describes the interface - the inputs and outputs.

The **entity** must be given a name, which may optionally be repeated at the end of the **entity**.

A —

B —

C —

D —

— F

```
entity AOI is
    ...
end AOI;
```

Glossary


Find

Copy

Help

Back



 


# The Design Entity

Design Entities

3 of 59

The **architecture** describes what is inside the block of hardware - its behaviour or structure. The **architecture** must also be given a **name**, which may optionally be repeated at the end of the **architecture**.

 An **entity** can have more than one **architecture**.




```
entity AOI is
    ...
end AOI;

architecture V1 of AOI is
    ...
begin
    ...
end V1;
```

Glossary Find Copy Help Back




 
 
# The Design Entity

The pins around the block of hardware are described as **ports** in the **entity**.


Each **port** is named in the **entity**, and is classified as **in** or **out**. **Ports** with the same classification can be listed together, separated by commas, as shown.




```
entity AOI is  
  port (A, B, C, D: in ...  
        F: out ...);  
end AOI;
```



 The name of the output **port** goes on the left hand side of the **assignment**.



 


# The Design Entity

Design Entities

6 of 59

 On the right hand side of the **signal assignment** is an **expression** which calculates the value of the output from the value of the inputs.



```
entity AOI is
  port (A, B, C, D: in ...
        F: out ...);
end AOI;

architecture V1 of AOI is
begin
  F <= not ((A and B) or (C and D));
end V1;
```

Glossary Find Copy Help Back






# The Design Entity

Design Entities

7 of 59

Each **port** has a data **type** which describes the kind of information which can pass through the **port**. This may seem odd, since it is clear that each port represents just one physical pin, but this will not always be the case.

 The type **STD\_LOGIC** indicates that each **port** carries just one digital logic value, either '0' or '1'. The value on each **port** can change over time.




```
entity AOI is
    port (A, B, C, D: in STD_LOGIC;
          F: out STD_LOGIC);
end AOI;

architecture V1 of AOI is
begin
    F <= not ((A and B) or (C and D));
end V1;
```

Glossary Find Copy Help Back





 


# The Design Entity

Design Entities

8 of 59

The type `STD_LOGIC` is defined in the package `STD_LOGIC_1164` on library `IEEE`.

 The two lines starting `library` and `use` appear at the top of many `entities`, and tell the VHDL compiler where to find the definition of `STD_LOGIC`.




```
library IEEE;
use IEEE.STD_LOGIC_1164.all;

entity AOI is
    port (A, B, C, D: in STD_LOGIC;
          F: out STD_LOGIC);
end AOI;

architecture V1 of AOI is
begin
    F <= not((A and B) or (C and D));
end V1;
```

Glossary Find Copy Help Back



 


# The Design Entity

Design Entities

9 of 59

Data **types** are often defined in a **package**.

 Confusingly, a VHDL **package** does NOT represent a physical package, but is just a language construct where common, shared definitions can be placed.




```
library IEEE;
use IEEE.STD_LOGIC_1164.all;

entity AOI is
    port (A, B, C, D: in STD_LOGIC;
          F: out STD_LOGIC);
end AOI;

architecture V1 of AOI is
begin
    F <= not((A and B) or (C and D));
end V1;
```

Glossary Find Copy Help Back



 


# The Design Entity

Design Entities

10 of 59

By the way, you may have noticed that some words are written in lower case, and others in upper case.

 
Well, VHDL is **not** case sensitive, so it does not actually matter! However, it is a good idea to have a convention, so in these examples built-in reserved keywords are in lower case, and user defined names in upper case.



```
library IEEE;  
use IEEE.STD_LOGIC_1164.all;  
  
entity AOI is  
    port (A, B, C, D: in STD_LOGIC;  
          F: out STD_LOGIC);  
end AOI;  
  
architecture V1 of AOI is  
begin  
    F <= not ((A and B) or (C and D));  
end V1;
```

Glossary Find Copy Help Back




 
 
# The Design Entity

Here is the complete **design entity**. Click on the hotwords for a further explanation of each detail of the VHDL description.

When you've finished, move on to the exercises that follow. If you have difficulty with an exercise, you should review the earlier part of the lesson before proceeding.




```
library IEEE;
use IEEE.STD_LOGIC_1164.all;

entity AOI is
    port (A, B, C, D: in STD_LOGIC;
          F: out STD_LOGIC);
end AOI;

architecture V1 of AOI is
begin
    F <= not((A and B) or (C and D));
end V1;
```

Glossary Find Copy Help Back



 

## Exercise 1

Design Entities

12 of 59

Using the mouse, sort the lines into the correct order by dragging them up and down.

Do not press the up arrow key!

Check Answer


Correct! Well done. Try the next exercise.

```
library IEEE;
use IEEE.STD_LOGIC_1164.all;
entity AOI is
    port (A, B, C, D: in STD_LOGIC;
          F: out STD_LOGIC);
end AOI;
architecture V1 of AOI is
begin
    F <= not ((A and B) or (C and D));
end V1;
```

Glossary Find Copy Help Back



The Answer

 

## Exercise 2

Design Entities

13 of 59


Drag and drop each VHDL term into the appropriate slot.

Correct.

architecture	= the internal function of a block of hardware
port	= a pin
std_logic	= a type representing one bit of information
design entity	= the complete definition of a block of hardware
entity	= the definition of the interface to a block of hardware
package	= a place to put common definitions

Glossary Find Copy Help Back



 


# Signals

Design Entities

14 of 59

 Let's now see how we can add internal connections to our **design entity**. We'll modify the AOI to include separate interconnected gates, instead of one boolean function.



Glossary


Find

Copy

Help

Back



 


# Signals

Design Entities

15 of 59

We're now going to construct a second alternative **architecture** named V2 for our AOI **entity**.

 The main reason for having **architectures** in VHDL is so that you can create more than one description for the same piece of hardware. This second variant of the AOI is named V2, although the name can be whatever you like.



```
architecture V2 of AOI is  
    ...  
begin  
    ...  
end V2;
```

Glossary

Find

Copy

Help

Back








# Signals

Design Entities

16 of 59

An internal connection is described in VHDL as a **signal** defined inside an **architecture**.

 Each **signal** has a **type**, and **signals** with the same **type** can be listed together.



```
architecture V2 of AOI is
    signal AB, CD, O: STD_LOGIC;
begin
    ...
end V2;
```

Glossary


Find

Copy

Help

Back



 


# Signals

Design Entities

17 of 59

The function of each gate is described by a concurrent **signal assignment**. The order in which the assignments are written has no effect on their behaviour.

 
Each **signal assignment** will be synthesized to the equivalent combinational logic gates, as shown in the diagram.



```
architecture V2 of AOI is
    signal AB, CD, O: STD_LOGIC;
begin
    AB <= A and B after 2 NS;
    CD <= C and D after 2 NS;
    O <= AB or CD after 2 NS;
    F <= not O after 1 NS;
end V2;
```

Glossary Find Copy Help Back



 

# Concurrent Assignments

Design Entities

18 of 59

A concurrent **signal assignment** is triggered by an **event** on a **signal**. An **event** is a change in value.

An **event** on the input **port** A would trigger the **assignment** to AB.



```
port (A, B, C, D: in STD_LOGIC;  
...  
AB <= A and B after 2 NS;
```

Glossary


Find

Copy

Help

Back



 


# Concurrent Assignments

Design Entities

19 of 59

 
The **signal assignment** first calculates the value of the **expression** on the right hand side.



```
AB <= A and B after 2 NS;
```

Glossary Find Copy Help Back



 


# Concurrent Assignments

Design Entities

20 of 59

The **signal assignment** then schedules a future **event** on the **signal** on the left hand side of the **assignment** to occur after the given delay.

 
The delay is very important for simulation, but not for synthesis. Synthesis tools ignore delays in **signal assignments**! Delay information for synthesis must be specified separately in the form of timing constraints.



```
AB <= A and B after 2 NS;
```

Glossary Find Copy Help Back



 


# Concurrent Assignments

Design Entities

21 of 59

After 2 NS have elapsed, the **event** on AB occurs, which triggers the **assignment** to O. An **event** is scheduled to occur on O after a further delay of 2 NS. That **event** in turn triggers the **assignment** to F.

 
The total delay from A to F is  $2 + 2 + 1 = 5$  NS.



```
AB <= A and B after 2 NS;  
CD <= C and D after 2 NS;  
O <= AB or CD after 2 NS;  
F <= not O after 1 NS;
```

Glossary Find Copy Help Back



 

## Exercise 3

Design Entities

22 of 59

If an event occurs on A at time 0 NS, at what time does F change value.  
(Type your answer in the box, then hit the Enter key.)

Correct. The event on A triggers the assignment to C, which then triggers the assignment to F. The 1st assignment to A does not contribute.


```
architecture V1 of Logic is
    signal A, C: Std_logic;
begin
    A <= not D after 1 NS;
    F <= C xor D after 2 NS;
    C <= A xor B after 4 NS;
end V1;
```

6 NS

Glossary Find Copy Help Back



The Answer

 


# Components

Design Entities

23 of 59

Let's now see how to build a hierarchy of **design entities**.

 We will take the AOI gate and connect it to an inverter to build a multiplexer. The **entity** is shown here.




```
library IEEE;
use IEEE.STD_LOGIC_1164.all;

entity MUX2 is
    port (SEL, A, B: in STD_LOGIC;
          F: out STD_LOGIC);
end MUX2;
```

Glossary Find Copy Help Back





 

# Components

Design Entities

24 of 59


Each lower level design entity must be declared as a **component** within the **architecture**. The **component declaration** repeats the **name** and the **ports** of the corresponding lower level **entity**.

A **component** is analogous to a chip socket - it creates an extra interface which allows more flexibility when building a hierarchical system out of its component parts.

```
architecture STRUCTURE of MUX2 is
    component INV
        port (A: in  STD_LOGIC;
              F: out STD_LOGIC);
    end component;
    component AOI
        port (A, B, C, D: in STD_LOGIC;
              F: out  STD_LOGIC);
    end component;
    ...
begin
    ...
end STRUCTURE;
```

Glossary Find Copy Help Back



 

# Components

Design Entities

25 of 59


Each **component** must now be **instantiated** within the **architecture**. The term **instantiation** may seem like obscure jargon, but the idea is very simple. An **instantiation** is VHDL jargon for a unique, concurrent copy of a **design entity**.

This **architecture** contains **instantiations** of the **components** INV and AOI.

```
architecture STRUCTURE of MUX2 is
  component INV
    port (A: in  STD_LOGIC;
          F: out STD_LOGIC);
  end component;
  component AOI
    port (A, E, C, D: in STD_LOGIC;
          F: out  STD_LOGIC);
  end component;
  signal SELB: STD_LOGIC;
begin
  G1: INV port map(SEL, SELB);
  G2: AOI port map(SEL, A, SELB, E, F);
end STRUCTURE;
```

Glossary Find Copy Help Back



 

# Components

Design Entities

26 of 59


In other words, having defined a piece of hardware as a **design entity**, an **instantiation** allows you to use that description as part of another higher level description.

What is more, you can use it as many times as you wish by writing lots of **instantiations**, each with its own **label**. The same **label** can only be used once in a particular **architecture**.

```
architecture STRUCTURE of MUX2 is
  component INV
    port (A: in  STD_LOGIC;
          F: out STD_LOGIC);
  end component;
  component AOI
    port (A, B, C, D: in STD_LOGIC;
          F: out  STD_LOGIC);
  end component;
  signal SELB: STD_LOGIC;
begin
  G1: INV port map(SEL, SELB);
  G2: AOI port map(SEL, A, SELB, B, F);
end STRUCTURE;
```

Glossary Find Copy Help Back



 


# Components

Design Entities

27 of 59


A picture is worth a thousand words, so they say! Let's illustrate our MUX2 example with a diagram.

 Click anywhere on the diagram with the mouse pointer and the appropriate VHDL term will appear in the Pop-up window! Note that **component instances** are equivalent to chips in sockets.



Glossary Find Copy Help Back



 

# Components

Design Entities


28 of 59

Now for the connections.

The **port map** makes the connections to **ports** on a **component instantiation** according to the order of the ports in the **component declaration**. So SELB, the third name in the **port map**, is connected to **port C**, the third **port** on the **component**.


architecture STRUCTURE of MUX2 is
 
```
...  
component AOI  
  port (A, B, C, D: in STD_LOGIC;  
        F: out STD_LOGIC);  
end component;  
...  
begin  
  ...  
  G2: AOI port map (SEL, A, SELB, B, F);  
end STRUCTURE;
```



Glossary Find Copy Help Back



 


# Components


The use of **components** is very important for synthesis, since it allows the hierarchy of the synthesized design to be controlled.


You can choose to synthesize your design as several separate blocks, thus steering the architecture of the design, or to "flatten" the design to a single level and allow the optimizer to change the architecture.

Hierarchical synthesis

 

Flat synthesis

 

 

# Components

Design Entities

30 of 59

In VHDL '93, there is an important change to the way hierarchy is described. You do not need **components**! It is possible to instantiate **design entities** directly, without using **components** as sockets! This makes the VHDL code much more straightforward and less verbose.

Once again, explore the diagram by pointing and clicking!


Entity

Architecture

```
G1: entity WORK.INV (ARCH)
    port map (SEL, SELB);
```

```
G2: entity WORK.AOI (V2)
    port map (SEL, A, SELB, B, F);
```

VHDL '93 only!

 

Glossary


Find

Copy

Help

Back



 

## Exercise 4

Design Entities

31 of 59

Use the mouse to drag the lines up and down into the correct order. There is only one correct answer.

Check Answer

Correct! Well done.


```
library IEEE;
use IEEE.STD_LOGIC_1164.all;
entity E is
    port (A: in STD_LOGIC;
          F: out STD_LOGIC);
end E;
architecture STRUCTURE of E is
    component C
        port (X: in STD_LOGIC;
              Y: out STD_LOGIC);
    end component;
begin
    G1: C port map (A, F);
end STRUCTURE;
```

Glossary Find Copy Help Back



The Answer



 

## Exercise 5

Design Entities

32 of 59

Drag and drop each of the VHDL terms into the appropriate slot.

Correct!

signal = a piece of wire

event = a change in the value on a piece of wire

instantiation = a specific chip socket


port map = the electrical connections to a specific chip socket

assignment = the thing that changes the value on a piece of wire

component = the footprint of a chip socket

Glossary Find Copy Help Back



 

## Exercise 6

Design Entities

33 of 59


Which port of the FullAdder is the signal Cout connected to in the instantiation labelled FA? (Type your answer in the box, then hit the Enter key.)

```
component FullAdder
    port (A, B, Cin: in Std_logic;
          Sum, Cout: out Std_logic);
end component;
```

```
FA: FullAdder
    port map (X, Y, Cout, A, B);
```

Glossary Find Copy Help Back



 

# Std\_logic\_vector

Design Entities

34 of 59

Now let's explore the **types** **Std\_logic** and **Std\_logic\_vector**. **Std\_logic** represents a single digital logic value. A value of this **type** is written in single quotes, as shown. The value 'U' means uninitialized, and 'X' means unknown.

A **Std\_logic\_vector** is a row of **Std\_logic** values, used to describe busses and vectors. **Std\_logic\_vector** is an **array** type.

```
signal E: STD_LOGIC;
```

```
...  
E <= '0';
```

```
...  
E <= '1';
```

```
...  
E <= 'X';
```

```
signal V: STD_LOGIC_VECTOR(7 downto 0);
```

V:

0	1	0	1	X	X	X	X
---	---	---	---	---	---	---	---

Glossary


Find

Copy

Help

Back



 


# Std\_logic\_vector

Design Entities

35 of 59

 The port SEL in this 4 to 1 multiplexer is a two bit array, described by using the type `Std_logic_vector`, and giving the width of the array.



```
library IEEE;
use IEEE.STD_LOGIC_1164.all;

entity MUX4 is
  port (
    SEL: in STD_LOGIC_VECTOR(1 downto 0);
    A, B, C, D: in STD_LOGIC;
    F: out STD_LOGIC);
end MUX4;
```

Glossary

Find

Copy

Help

Back





# Std\_logic\_vector

Design Entities

36 of 59

The range of an **array** can be defined in either ascending or descending order, using the keywords **to** or **downto**. This implies the order in which the bits of the **array** are numbered, but actually says nothing about which bit is the most significant.

Descending


```
signal V: STD_LOGIC_VECTOR(7 downto 0);
```

```
signal W: STD_LOGIC_VECTOR(0 to 7);
```

Ascending

Glossary Find Copy Help Back



 

# Std\_logic\_vector

Design Entities

37 of 59

A value of type `Std_logic_vector` is written as a text `string` enclosed in double quotes. The length of the `string` must match the number of `elements` defined in the `type`.


Array of 8 elements

```
signal V: STD_LOGIC_VECTOR(7 downto 0);  
...  
V <= "0101XXXX";
```

String of 8 characters

Glossary Find Copy Help Back



 


# Std\_logic\_vector

Individual bits within an **array** can be accessed using an **indexed name**, which is a **name** followed by an **index expression** in parenthesis.

```
signal V: STD_LOGIC_VECTOR(7 downto 0);  
  
...  
  
V(7) <= V(6);
```

Copy bit 6 into bit 7

 

# Std\_logic\_vector

Design Entities

39 of 59


Each **element** of a **Std\_logic\_vector** is actually a value of **type Std\_logic**, so its value has to be written in single quotes.

```
signal V: STD_LOGIC_VECTOR(7 downto 0);  
  
...  
  
V(7) <= '1';
```

Glossary Find Copy Help Back





 

# Std\_logic\_vector

Design Entities

40 of 59

It is also possible to access part of an **array**, rather than the entire **array** or a single **element** of the **array**.

Accessing part of an **array** is called a **slice name** in VHDL jargon.

**Array elements** are copied from left to right, such that the leftmost bit on the right of the **assignment** is copied into the leftmost bit on the left of the **assignment**.

```
signal V: STD_LOGIC_VECTOR(7 downto 0);  
signal W: STD_LOGIC_VECTOR(0 to 3);
```

...

```
W <= V(7 downto 4);
```


V(7) copied into W(0), V(6) into W(1) etc

```
V(3 downto 0) <= "01XZ";
```

leaving V(3) = '0', V(2) = '1' etc

Glossary Find Copy Help Back



 

## Exercise 7

Design Entities

41 of 59

Drag and drop each of the VHDL expressions into the appropriate slot. There is only one overall solution in which every item is correct.

'0'

"11"

"0000"

0

2

3

```
signal P: Std_logic_vector(3 downto 0);
```

```
P <= _____ ;
```

```
P ( _____ downto _____ ) <= _____ ;
```

```
P ( _____ ) <= _____ ;
```

Glossary


Find

Copy

Help

Back



 

# Test Benches



Design Entities

42 of 59

A VHDL simulation requires not only the hardware design described in VHDL, but also test vectors described in VHDL.


A **design entity** which provides a simulation environment for the hardware design is commonly known as a **test bench** in the VHDL world.

entity TEST\_MUX4

  

Glossary Find Copy Help Back



 

# Test Benches



Design Entities

43 of 59

A VHDL **test bench** makes an **instantiation** of the **design entity** at the top of the hardware design hierarchy, and contains VHDL code to apply test vectors to the inputs of the design.


The **test bench architecture** may also include VHDL code to analyze the outputs of the design. **Test benches** are never synthesized, of course!

entity TEST\_MUX4

  

Glossary Find Copy Help Back



 

# Test Benches

Design Entities

44 of 59



Let's look at a **test bench** for the **design entity** MUX4.

The **entity** for a **test bench** is usually empty. This is important, as many VHDL simulators do not permit **ports** on top level **entities**.

```
library IEEE;  
use IEEE.STD_LOGIC_1164.all;
```


```
entity TEST_MUX4 is  
end;
```

Empty!

  

Glossary Find Copy Help Back



 

# Test Benches

Design Entities

45 of 59



The **test bench** architecture includes a **component declaration** corresponding to the MUX4 **design entity**, because we want the MUX4 as a lower level hierarchical block in the **test bench**.

The **component declaration** repeats the **ports** from the **entity**.

architecture BENCH of TEST\_MUX4 is

```
component MUX4
  port (SEL: in
        STD_LOGIC_VECTOR(1 downto 0);
        A, B, C, D: in STD_LOGIC;
        E: out STD_LOGIC);
end component;
```

```
...
begin
  ...
end BENCH;
```

  

Glossary


Find

Copy

Help

Back



 

# Test Benches

Design Entities



46 of 59

We also need an **instantiation** of the component. This is critical, because it is the **instantiation** that actually creates a copy of the MUX4, not the **component declaration**.

The **instantiation** includes a **port map** to connect up the **ports** of the **component**.

architecture BENCH of TEST\_MUX4 is
  
```
    component MUX4
      port (SEL: in STD_LOGIC_VECTOR
              (1 downto 0);
            A, B, C, D: in STD_LOGIC;
            F          : out STD_LOGIC);
    end component;
    ...
begin
    ...
    M: MUX4 port map(SEL, A, B, C, D, F);
end BENCH;
```



Glossary


Find

Copy

Help

Back



 

# Test Benches

Design Entities



47 of 59

The **signals** that are connected to the **ports** of the MUX4 must also be declared in the **architecture**. These **signals** represent internal connections within the **test bench**.

```
architecture BENCH of TEST_MUX4 is
...
  signal SEL:
    STD_LOGIC_VECTOR(1 downto 0);
  signal A, B, C, D, F: STD_LOGIC;

begin
  ...
  M: MUX4 port map(SEL, A, B, C, D, F);


end BENCH;
```

  

Glossary Find Copy Help Back





 

# Test Benches

Design Entities

48 of 59

Finally, the **test bench** must generate the test vectors to be applied to the input **ports** of the MUX4. This is done with concurrent **signal assignments** to the **signals** declared in the **architecture**.

Each **signal assignment** creates several **events** on a **signal** at the times given in the assignment.

architecture BENCH of TEST\_MUX4 is

...

begin

```
SEL <= "00", "01" after 30 NS,  
      "10" after 60 NS, "11" after 90 NS,  
      "XX" after 120 NS, "00" after 130 NS;
```

```
A <= 'X',  
     '0' after 10 NS,  
     '1' after 20 NS;
```



```
B <= 'X',  
     '0' after 40 NS,  
     '1' after 50 NS;
```

```
C <= 'X',  
     '0' after 70 NS,  
     '1' after 80 NS;
```

```
D <= 'X',  
     '0' after 100 NS,  
     '1' after 110 NS;
```


...

end BENCH;

  

Glossary Find Copy Help Back



 

# Test Benches


Design Entities

49 of 59

In order to clarify the meaning of these **signal assignments**, let's try to visualize what these test vectors look like graphically. This is shown in the diagram opposite.

```
SEL <= "00", "01" after 30 NS,  
      "10" after 60 NS, "11" after 90 NS,  
      "XX" after 120 NS, "00" after 130 NS;
```
 
```
A <= 'X', '0' after 10 NS,  
      '1' after 20 NS;  
B <= 'X', '0' after 40 NS,  
      '1' after 50 NS;  
C <= 'X', '0' after 70 NS,  
      '1' after 80 NS;
```



Glossary


Find

Copy

Help

Back



 

## Exercise 8

Design Entities

50 of 59

Drag and drop the fragments of VHDL code into the appropriate slots in the architecture to make a complete test bench.

```
library IEEE; use IEEE.STD_LOGIC_1164.all;  
entity TestBench is
```

```
end;
```

```
architecture V1 of TestBench is
```

```
begin
```

```
end;
```

```
A <= '0',  
      '1' after 10 NS;
```

```
component C  
port(P:in Std_logic;Q:out Std_Logic);  
end component;
```

```
L: C port map (A, F);
```

```
signal A: Std_logic;  
signal F: Std_logic;
```

```
port (A: in Std_logic;  
      F: out Std_logic);
```

Glossary


Find

Copy

Help

Back



 

# Configurations



Design Entities

51 of 59

So, a design written in VHDL consists of many **design entities** (representing hierarchical blocks), and also a few **packages** (containing common definitions).


In order to **simulate** or **synthesize** the hierarchy, we must select the **entity** and **architecture** to be used for each **component instantiation** throughout the hierarchy.

entity TEST\_MUX4

  

Glossary Find Copy Help Back



 

# Configurations

Design Entities

52 of 59


VHDL contains a construct for selecting which **entities** and **architectures** are to be used. This is called the **configuration**.

A **configuration** is a separate piece of VHDL text, and must be given a **name** which optionally may be repeated at the end of the **configuration**.

```
configuration CFG_MUX4 of TEST_MUX4 is
  for BENCH
  end for;
end CFG_MUX4;
```

Glossary Find Copy Help Back



 

# Configurations

Design Entities

53 of 59

A **configuration** always belongs to a specific **entity**, in this case the top level **test bench** TEST\_MUX4.


```
entity TEST_MUX4 is  
end;
```

...

```
configuration CFG_MUX4 of TEST_MUX4 is  
  for BENCH  
    end for;  
end CFG_MUX4;
```

Glossary Find Copy Help Back



 

# Configurations

Design Entities

54 of 59

A **configuration** always configures a specific **architecture**, which is named immediately inside the **configuration**. BENCH is the **architecture** of entity TEST\_MUX4.

Note that it is the **test bench** being configured, not the design under test. BENCH is the **architecture** of the **test bench**.

```
architecture BENCH of TEST_MUX4 is  
    ...  
end;
```

```
configuration CFG_MUX4 of TEST_MUX4 is  
    for BENCH  
    end for;  
end CFG_MUX4;
```

Glossary


Find

Copy

Help

Back



 

# Configurations

Design Entities

55 of 59

The VHDL standard defines some default rules for how **component instantiations** are to be configured in the absence of explicit instructions.

By default, an **entity** with the same name and **ports** as the **component** is used, together with the most recently compiled **architecture**.

```
component MUX4
  port (SEL: in
        STD_LOGIC_VECTOR(1 downto 0);
        A, B, C, D: in STD_LOGIC;
        E: out  STD_LOGIC);
end component;
```

```
entity MUX4 is
  port (SEL: in
        STD_LOGIC_VECTOR(1 downto 0);
        A, B, C, D: in STD_LOGIC;
        E: out  STD_LOGIC);
end MUX4;
```

Glossary

Find


Copy

Help

Back





 

# Configurations

Design Entities

56 of 59

Despite these rules, many VHDL tools insist that the minimal **configuration** declaration shown here must exist for the top level **design entity** in the hierarchy!

```
configuration CFG_MUX4 of TEST_MUX4 is
    for BENCH
        end for;
end CFG_MUX4;
```

Glossary


Find

Copy

Help

Back



 

# Configurations

Design Entities

57 of 59

Some VHDL tools go further, and insist that any **entities** to be used are made directly visible to the compiler in the **configuration declaration**.

The **use clause** shown makes the **entity** MUX4 visible, so it can be used for the MUX4 **component** in **architecture** BENCH.

This completes our tour of **design entities**.

```
use WORK.all;  
configuration CFG_MUX4 of TEST_MUX4 is  
  for BENCH  
  end for;  
end CFG_MUX4;
```

Glossary


Find

Copy

Help

Back




 

 
## Exercise 9

Choose the definition which most accurately describes the purpose of a configuration.


Correct! The "minimal" configurations we've seen use the default rules to select entities and architectures.



 To define the functionality of the design hierarchy



 To define the connections between components



To tell the compiler where to find the architectures available for an entity



To define which entities and architectures are used in the design hierarchy

Glossary


Find

Copy

Help

Back



 

## Exercise 10

Design Entities

59 of 59

Assemble a minimal configuration for the given architecture out of the parts provided! Note that some of the parts are not used!

Incorrect! Try again.

```
entity Top is  
end Top;
```

```
architecture Bench of Top is  
  component Main
```

```
    ...
```

```
  end component;
```

```
  ...
```

```
begin
```

```
  ...
```

```
end Bench;
```

Bench

for

is

Main

Main

configuration

Cfg

of

Top

is

for

Bench

of

end

Top

;

end

Cfg

;

Glossary

Find

Copy

Help

Back

